

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## FINAL EXAMINATION

TRIMESTER 2, 2015/2016

**DET5078 – ANALOG ELECTRONICS 2**  
(Diploma in Electronics Engineering)

11 MARCH 2016  
9 AM – 11 AM  
(2 Hours)

---

### INSTRUCTIONS TO STUDENTS

1. This booklet consists of 5 pages with **5 questions** only excluding the cover.
2. Attempt **ALL** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please write all your answers in the answer booklet provided. All necessary working **MUST** be shown in the answer booklet.

**QUESTION 1 [20 marks]**

- (a) List down **THREE** advantages and **TWO** disadvantages of JFET. (5 marks)
- (b) Based on the Figure 1(a) below, **explain** in detail the biasing process to TURN ON a NPN Enhancement Mode MOSFET. (5 marks)

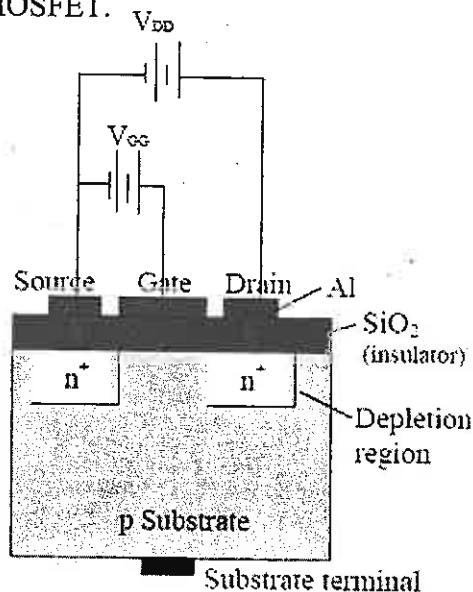


Figure 1(a)

- (c) A JFET transistor circuit is shown in Figure 1(b):

Given  $R_D = 5K\Omega$ ,  $R_G = 1M\Omega$ ,  $V_{DD} = 16V$ ,  $V_{GG} = 5V$ ,  $I_{DSS} = 10mA$  and  $V_p = -8V$ , find the following:

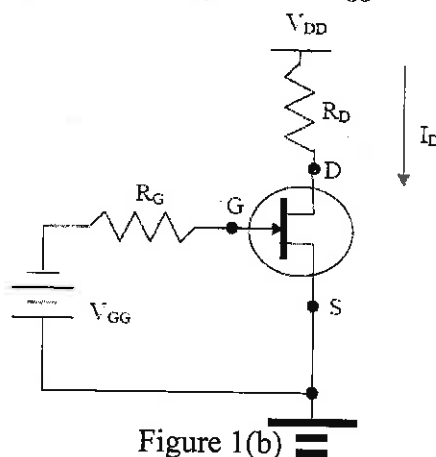


Figure 1(b)

- (i)  $V_{GSQ}$  and  $I_{DQ}$  (4 marks)
- (ii)  $V_{DS}$  and  $V_D$  (4 marks)
- (iii)  $V_G$  and  $V_S$  (2 marks)

Continued .....

**QUESTION 2 [20 marks]**

- (a) Explain the term “biasing a transistor”. (3 marks)
- (b) Miller Theorem is used in constructing a BJT or FET high frequency model. Briefly explain the theorem with aid of an illustration. (7 marks)
- (c) Figure 2 shows a high frequency model of a FET Common Source Amplifier.

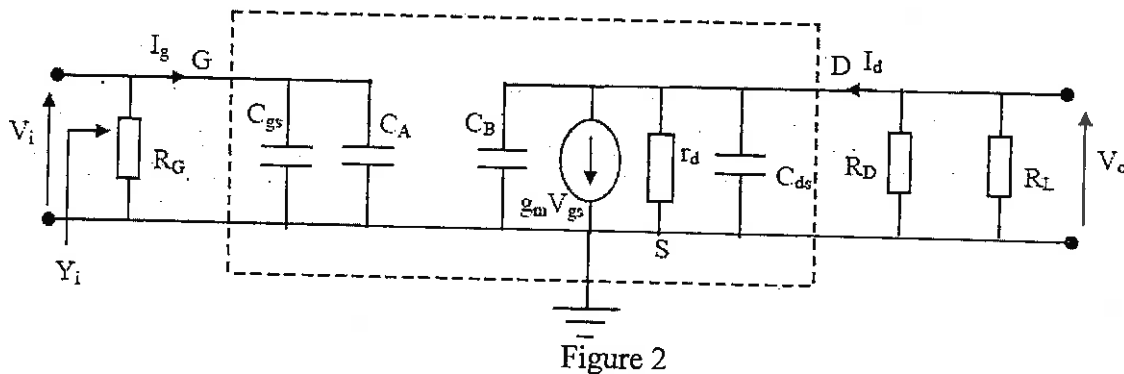


Figure 2

It has a  $R_G = 1\text{M}\Omega$ ,  $R_D = 50\text{ k}\Omega$ ,  $R_L = 6\text{ k}\Omega$  and operates up to 50 kHz. The FET parameters are  $g_m = 5\text{ mA/V}$ ,  $r_d = 50\text{ k}\Omega$ ,  $C_{gs} = 3\text{ pF}$ ,  $C_{ds} = C_{gd} = 1\text{ pF}$ . The coupling and bypass capacitors have large values of capacitance. Calculate the following:

- $Y_{gs}$  (1 mark)
- $Y_{ds}$  (1 mark)
- $G_G$  (1 mark)
- $G_D$  (1 mark)
- $G_L$  (1 mark)
- $g_d$  (1 mark)
- $|A_v|$  (4 marks)

Hint:

$$\begin{aligned}
 G_G &= 1/R_G, & G_D &= 1/R_D, & G_L &= 1/R_L, & g_d &= 1/r_d \\
 Y_{gs} &= j\omega C_{gs}, & Y_{ds} &= j\omega C_{ds}, & Y_{gd} &= j\omega C_{gd} \\
 Y_A &= Y_{gd}(1 - A_v), & Y_B &= Y_{gd}(1 - 1/A_v) & Y_A &= j\omega C_A, & Y_B &= j\omega C_B \\
 C_A &= C_{gd}(1 - A_v), & C_B &= C_{gd}(1 - 1/A_v)
 \end{aligned}$$

$$A_v = \frac{-g_m + Y_{gd}}{Y_{gd} + g_d + Y_{ds} + G_D + G_L}$$

Continued .....

**QUESTION 3 [20 marks]**

(a) An output waveform of a Class A amplifier is not an exact replica of the input signal waveform due to various types of distortion. Briefly explain the types of distortion below:

- (i) Amplitude Distortion (2 marks)
- (ii) Frequency Distortion (2 marks)
- (iii) Phase Shift Distortion (2 marks)

(b) Figure 3 shows an output waveform of an amplifier.

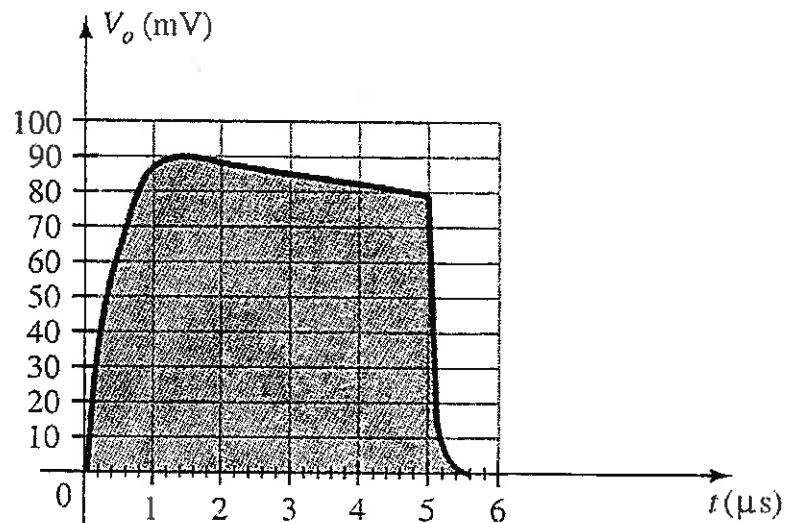


Figure 3

The input of the amplifier is a 20mV, 180kHz square wave signal. Based on Figure 3, calculate for the following parameters:

- (i) Upper cutoff frequency (5 marks)
- (ii) Lower cutoff frequency (4 marks)

(c) A type of RC circuit has a critical frequency at  $f_c = 888$  Hz, above which the attenuation is approaching 0 dB. Determine the dB attenuation at 88.8 Hz. (5 marks)

Continued .....

**QUESTION 4 [20 marks]**

- (a) Based on the Figure 4(a), **explain** in detail and **illustrate** a waveform for a type of distortion called “crossover distortion” which is experienced by a Class B amplifier.

(10 marks)

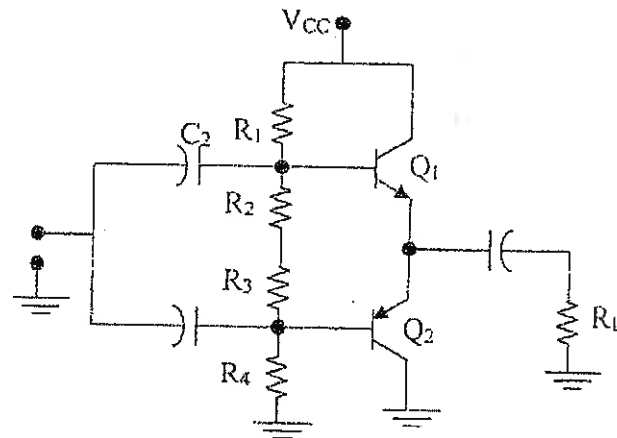


Figure 4(a)

- (b) Figure 4(b) shows a class B amplifier circuit.

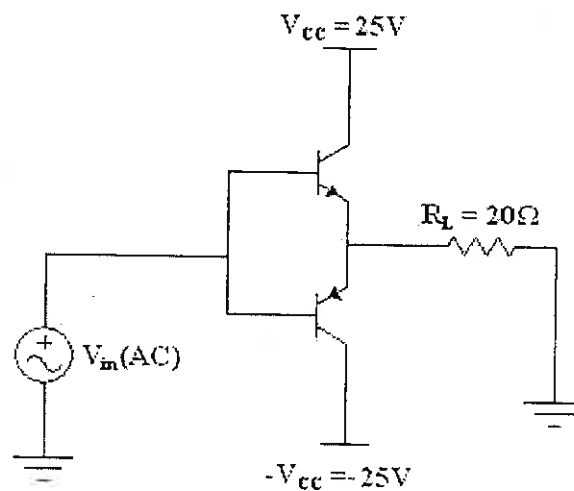


Figure 4(b)

The Class B amplifier provides 20V peak signal to a  $20\Omega$  load. Find the following:

- |                          |           |
|--------------------------|-----------|
| (i) Input power          | (6 marks) |
| (ii) Output power        | (2 marks) |
| (iii) Circuit efficiency | (2 marks) |

**Continued .....**

**QUESTION 5 [20 marks]**

- (a) Based on the below Schmitt Trigger circuit that would exhibit switching characteristics as shown in Figure 5 with  $R_{f1} = 3k\Omega$ ,  $R_{f2} = 7k\Omega$ ,  $R_i = 5k\Omega$  and supply voltages are  $\pm 12V$ . Assume that the load resistance is greater than  $2k\Omega$ .

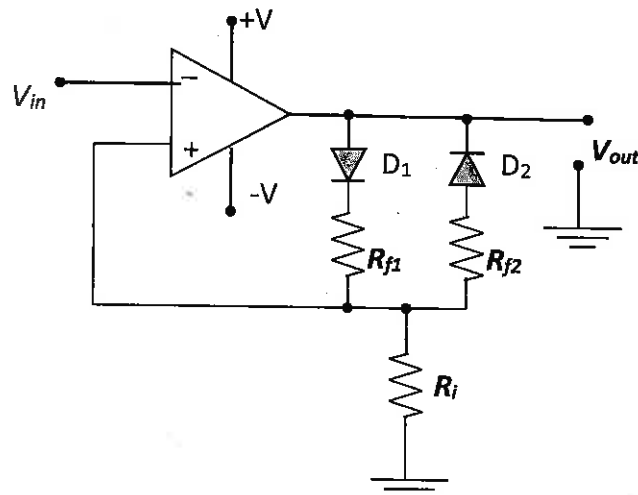


Figure 5

- (i) State the type of the Schmitt trigger (1 mark)
  - (ii) Determine the UTP and LTP (6 marks)
  - (iii) Sketch the input signal and output signal if input signal  $V_{in} = 8\sin(\pi t)$  is applied to the Schmitt Trigger in Figure 5. (4 marks)
- (b) Briefly explain about astable, monostable and bistable multivibrators. (6 marks)
- (c) Name THREE applications of the Astable Multivibrator. (3 marks)

**End of Page.**